

Final Assessment Test (FAT) – November/December 2022

Programme	B.Tech.	Semester	Fall Semester 2022-23
Course Title	DIGITAL SYSTEMS DESIGN	Course Code	BECE102L
Faculty Name	Prof. Sasithradevi A	Slot	F2+TF2
		Class Nbr	CH2022231001903
Time	3 Hours	Max. Marks	100
Answer ALL the Questions			

Section A (1 X 10 Marks)

Answer All questions

1. Perform multiplication of $(1010)_2 \times (111)_2$ using unsigned array multiplier and draw the equivalent logic diagram for 4x3 Array Multiplier. [10]

Section B (6 X 15 Marks)

Answer All questions

2. (a) Simplify the following function $F(A, B, C, D) = \pi(3, 4, 5, 6, 7, 10, 11, 14, 15)$ using K- Map. [15]
Also, implement the simplified expression using NOR gates only. (10 Marks)
(b) Implement the following Boolean function $out = (D + A(B + C))'$ using CMOS logic. (5 Marks)
3. In the given Verilog code, identify and debug the errors. Obtain the truth table and draw the logic diagram for the same. Also, explain the functionality of the design involved. [15]

```
module decoder(binary_in, decoder_out, enable)
```

```
input [3:0] binary_in;
```

```
input enable ;
```

```
output [15:0] decoderout
```

```
always @ (enable or binary)
```

```
begin
```

```
decoder_out = 0
```

```
if (enable) begin
```

```
case (binary_in)
```

```
4'h0 : decoder_out = 16'h0001; 4'h1 : decoder_out = 16'h0002;
```

```
4'h2 : decoder_out = 16'h0004; 4'h3 : decoder_out = 16'h0008;
```

```
4'h4 : decoder_out = 16'h0010; 4'h5 : decoder_out = 16'h0020;
```

```
4'h6 : decoder_out = 16'h0040; 4'h7 : decoder_out = 16'h0080;
```

```
4'h8 : decoder_out = 16'h0100; 4'h9 : decoder_out = 16'h0200;
```

```
4'hA : decoder_out = 16'h0400; 4'hB : decoder_out = 16'h0800;
```

```
4'hC : decoder_out = 16'h1000; 4'hD : decoder_out = 16'h2000;
```

```
4'hE : decoder_out = 16'h4000; 4'hF : decoder_out = 16'h8000;
```

```
end case
```

```
end
```

```
end module
```

4. Design a partially simplified Arithmetic Logic Unit (ALU) using basic logic gates which is capable of performing 1-bit arithmetic subtraction with the inclusion of borrow as an additional input. Implement the obtained logical expressions for difference and borrow using a suitable demultiplexer. [15]
5. Consider a smart parking system in a super market which indicates the number of free parking lots , out of which 8 parking lots are indicated as available in the display unit. Whenever the car enters into the super market premises , it will be identified by an IR sensor and the signal is sent to the control unit to decrement the available parking lot by one. Similarly, if any car leaves the supermarket premises, then increment the available parking lot by one. Design an appropriate control circuit which performs increment and decrement operations using T-Flip flop. [15]
6. Design Mealy sequence detector (Non Overlapping) to detect a sequence 1010 using D flipflop. [15]
7. (a) Implement the Boolean expression $Y = AB' + BC + AC'$ using (10 Marks) [15]
(i) Programmable Logic Array (PLA) and
(ii) Programmable Array Logic (PAL)
(b) Discuss about the difference between CPLD and FPGA. (5 Marks)

