

Reg. No.:

Name :



VIT


Vellore Institute of Technology

(Declared to be University under section 3 of UGC Act, 1956)

Continuous Assessment Test I – March 2023

Programme	B.Tech	Semester	WS 2022-23
Course	Digital System Design	Code	BECE102L
		Class Nbr	CH2022232300126
Faculty	Dr Gargi Raina	Slot	D1 + TD1
Time	90 Minutes	Max. Marks	50

Answer ALL the questions

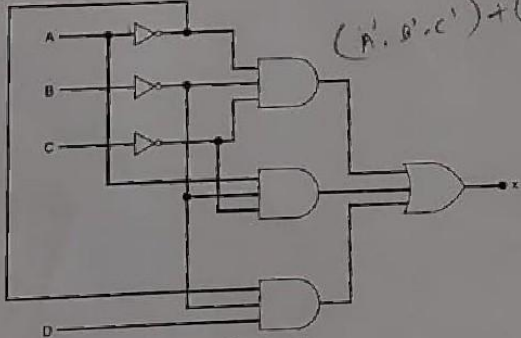Q.No.	Sub-division	Question Text	Marks
1.		A logic 'voter' circuit has 4 inputs a, b, c, d and one output v . The output is to be logic 1 if any 3 or all 4 inputs are at logic 1. Draw a truth table map for each input and hence write down the simplified Boolean equations using K-Map method of reduction. Design a circuit using NOR gates to satisfy this requirement.	[10]
2.		Draw a CMOS logic circuit for the given expression. (Assume both true and complementary inputs are available) $F = (A + \bar{C}D)(\bar{A} + B)$.	[5]
3.		Write the Boolean expression for output x in Figure 1. Determine the value of x for all possible input conditions in a truth table. 	[5]
4.	i. ii.	Simplify the given function $F1 = \sum (1, 5, 6, 7, 11, 12, 13, 15)$ For the original and the simplified expression, write the Verilog HDL code using dataflow modelling.	[5] + [5]
5.		Write a gate level Verilog code for the schematic shown in Figure 2 and write a test bench for the same.	[10]

 


Figure 2

Design a 4:2 priority encoder. Also discuss the differences between encoder and priority encoder?

[10]

Total Marks

[50]

$$I_0 + I_1 I_3'$$



$$I_0 + I_2$$

