

A pink, rounded rectangular button with a slight 3D effect and a green shadow, tilted at an angle. It is centered on a black rectangular background. The entire scene is framed by a white border with rounded corners.

COUNTERS

COUNTERS

TYPES OF COUNTER

- ❑ Flip-Flops can be connected together to perform counting operations. Such a group of Flip-Flops is a **counter**.
- ❑ The number of Flip-Flops used and the way in which they are connected determine the number of states (called the modulus)
- ❑ Counters are classified into two broad categories according to the way they are clocked:
 - Asynchronous counters
 - Synchronous counters.

COUNTERS

TYPES OF COUNTER

- ❑ In asynchronous (ripple) counters, the first Flip-Flop is clocked by the external clock pulse and then each successive Flip-Flop is clocked by the output of the preceding Flip-Flop.
- ❑ In synchronous counters, the clock input is connected to all of the Flip-Flops so that they are clocked simultaneously.
- ❑ Within each of these two categories, counters are classified primarily by the type of sequence, the number of states, or the number of Flip-Flops in the counter.


COUNTERS

SYNC. Vs ASYNC. COUNTER

S.No	Asynchronous (ripple) counter	Synchronous counter
1	All the Flip-Flops are not clocked simultaneously.	All the Flip-Flops are clocked simultaneously.
2	The delay times of all Flip-Flops are added. Therefore there is considerable propagation delay.	There is minimum propagation delay.
3	Speed of operation is low	Speed of operation is high.
4	Logic circuit is very simple even for more number of states.	Design involves complex logic circuit as number of state increases.
5	Minimum numbers of logic devices are needed.	The number of logic devices is more than ripple counters.
6	Cheaper than synchronous counters.	Costlier than ripple counters.

COUNTERS


2-BIT SYNC. UP COUNTER

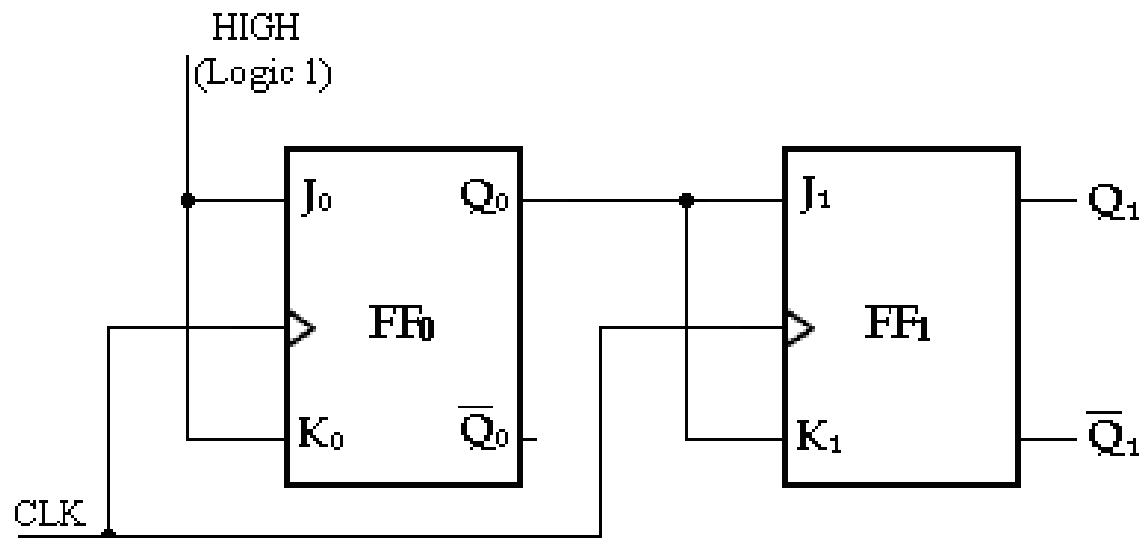

2-Bit Synchronous Binary Counter

COUNTERS

2-BIT SYNC. UP COUNTER

 

Timing diagram

COUNTERS

Design steps of synchronous counter

- Find the number of flip flops using $2^n \geq N$, where N is the number of states and n is the number of flip flops
- Choose the type of flip flop
- Draw the state diagram of the counter
- Draw the excitation table of the selected flip flop and determine the excitation table for the counter
- Use K-map to derive the flip flop input functions

COUNTERS

Design steps of synchronous counter

Design 3-bit synchronous up counter using [JK flip flops](#).

Step 1: Find the number of flip flops.

A flip flop stores only one bit, hence for a 3 bit counter, 3 flip flops($n=3$) are needed to design the counter.

Number of states = $2^n = 2^3 = 8$ states

Step 2: Choose the type of flip flop.

Since the type of flip flop is given in the problem, let us use JK flip flops.

Step 3: Write the sequence of the counter

000, 001, 010, 011, 100, 101, 110, 111

Obtain excitation table for the counter.

- We know, the [excitation table](#) for JK flip flop
- Excitation table for the 3-bit synchronous counter is determined from the excitation table of JK flip flop

COUNTERS

Design steps of synchronous counter

[Excitation table](#) for JK flip flop

Clock	Present State			Next State			Flip flop Inputs					
	Q_C	Q_B	Q_A	Q_{C+1}	Q_{B+1}	Q_{A+1}	J_C	K_C	J_B	K_B	J_A	K_A
1	0	0	0	0	0	1	0	X	0	X	1	X
2	0	0	1	0	1	0	0	X	1	X	X	1
3	0	1	0	0	1	1	0	X	X	0	1	X
4	0	1	1	1	0	0	1	X	X	1	X	1
5	1	0	0	1	0	1	X	0	0	X	1	X
6	1	0	1	1	1	0	X	0	1	X	X	1
7	1	1	0	1	1	1	X	0	X	0	1	X
8	1	1	1	0	0	0	X	1	X	1	X	1

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

COUNTERS

Design steps of synchronous counter

Step 5: Derive the flip flop input functions

For J_c

$Q_3 Q_A$ Q_c	00	01	11	10
0	0	0	1	0
1	X	X	X	X

$$J_c = Q_3 Q_A$$

For K_c

$Q_3 Q_A$ Q_c	00	01	11	10
0	X	X	X	X
1	0	0	1	0

$$K_c = Q_3 Q_A$$

For J_B

$Q_3 Q_A$ Q_c	00	01	11	10
0	0	1	X	X
1	0	1	X	X

$$J_B = Q_A$$

For K_B

$Q_3 Q_A$ Q_c	00	01	11	10
0	X	X	1	0
1	X	X	1	0

$$K_B = Q_A$$

For J_A

$Q_3 Q_A$ Q_c	00	01	11	10
0	1	X	X	1
1	1	X	X	1

$$J_A = 1$$

For K_A


$Q_3 Q_A$ Q_c	00	01	11	10
0	X	1	1	X
1	X	1	1	X

$$K_A = 1$$

COUNTERS


Design steps of synchronous counter

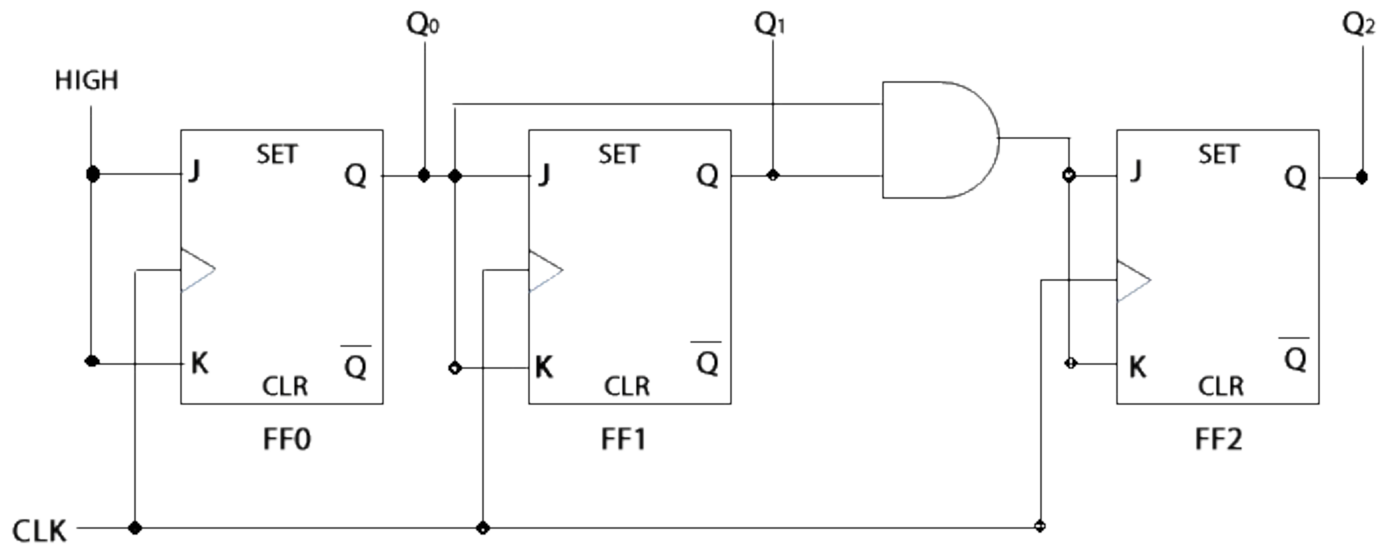Step 6: Draw the logic diagram of the counter.



COUNTERS


3-BIT SYNC. UP COUNTER

 

Timing diagram

COUNTERS


4-BIT SYNC. UP COUNTER

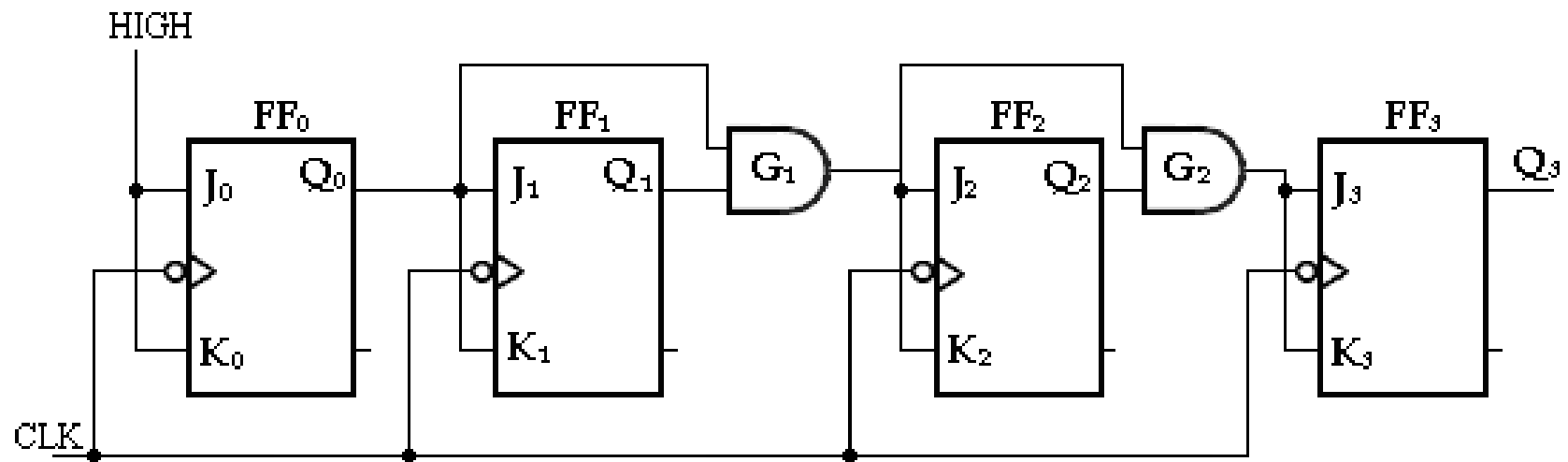

4-Bit Synchronous Binary Counter


COUNTERS

4-BIT SYNC. UP COUNTER

 

COUNTERS


2-BIT ASYNC. UP COUNTER

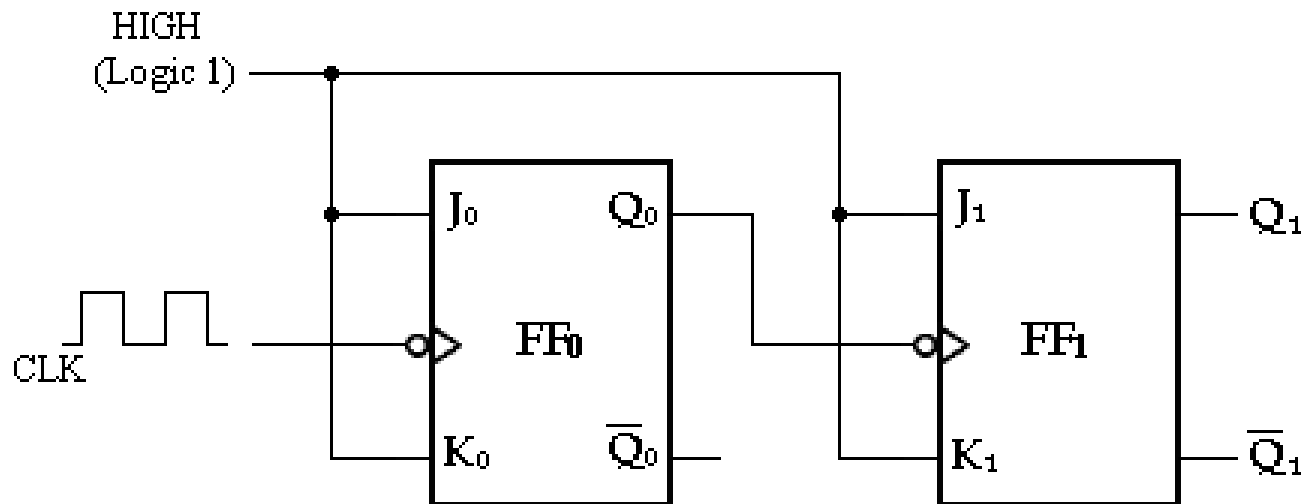

2-Bit Asynchronous Binary Counter

COUNTERS


2-BIT ASYNC. UP COUNTER

 

Timing diagram for 2-bit counter

COUNTERS


3-BIT ASYNC. UP COUNTER

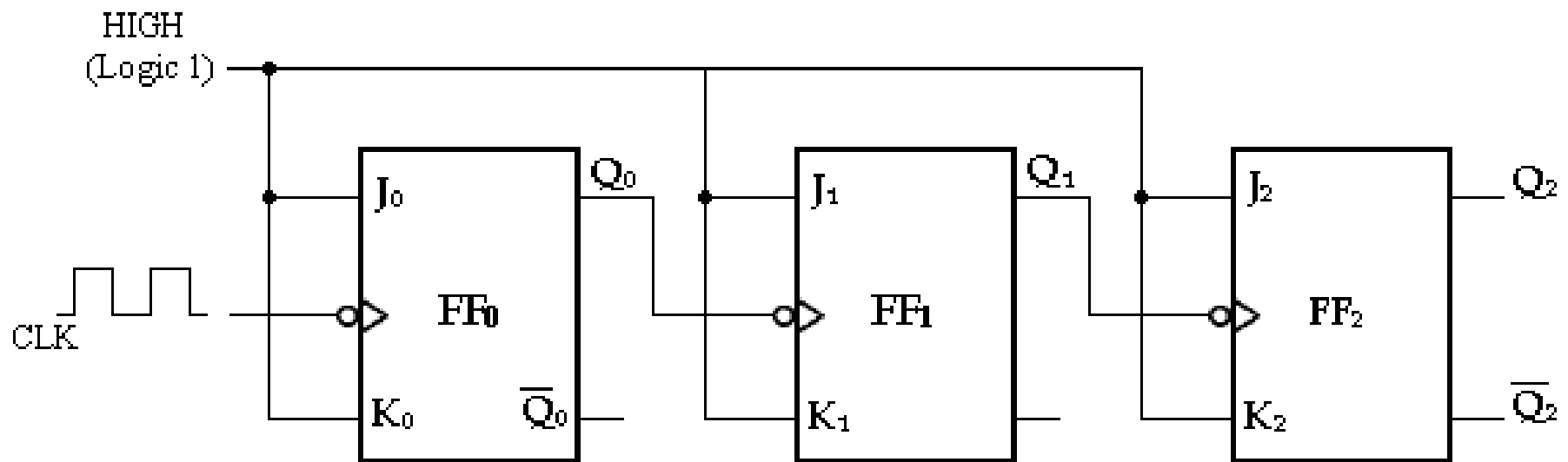

3-Bit Asynchronous Binary Counter

COUNTERS


3-BIT ASYNC. UP COUNTER

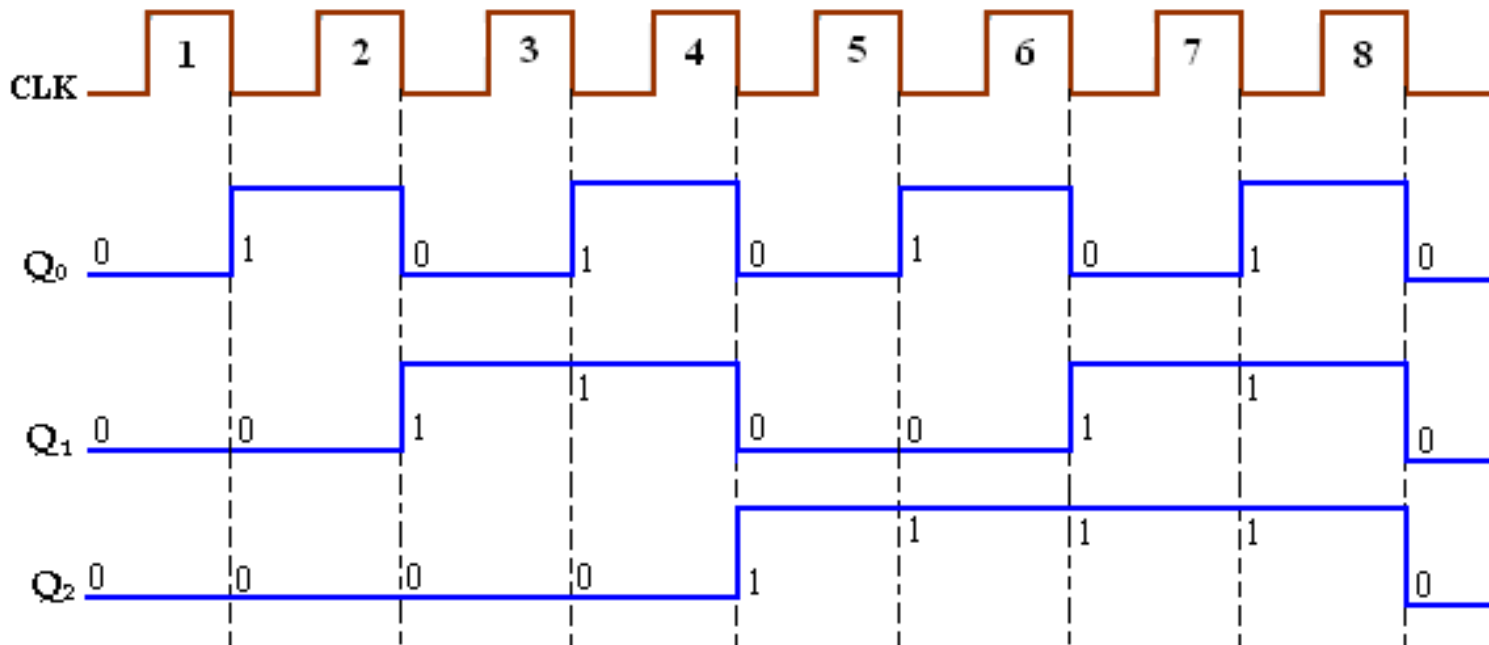

Timing diagram


COUNTERS

4-BIT ASYNC. UP COUNTER

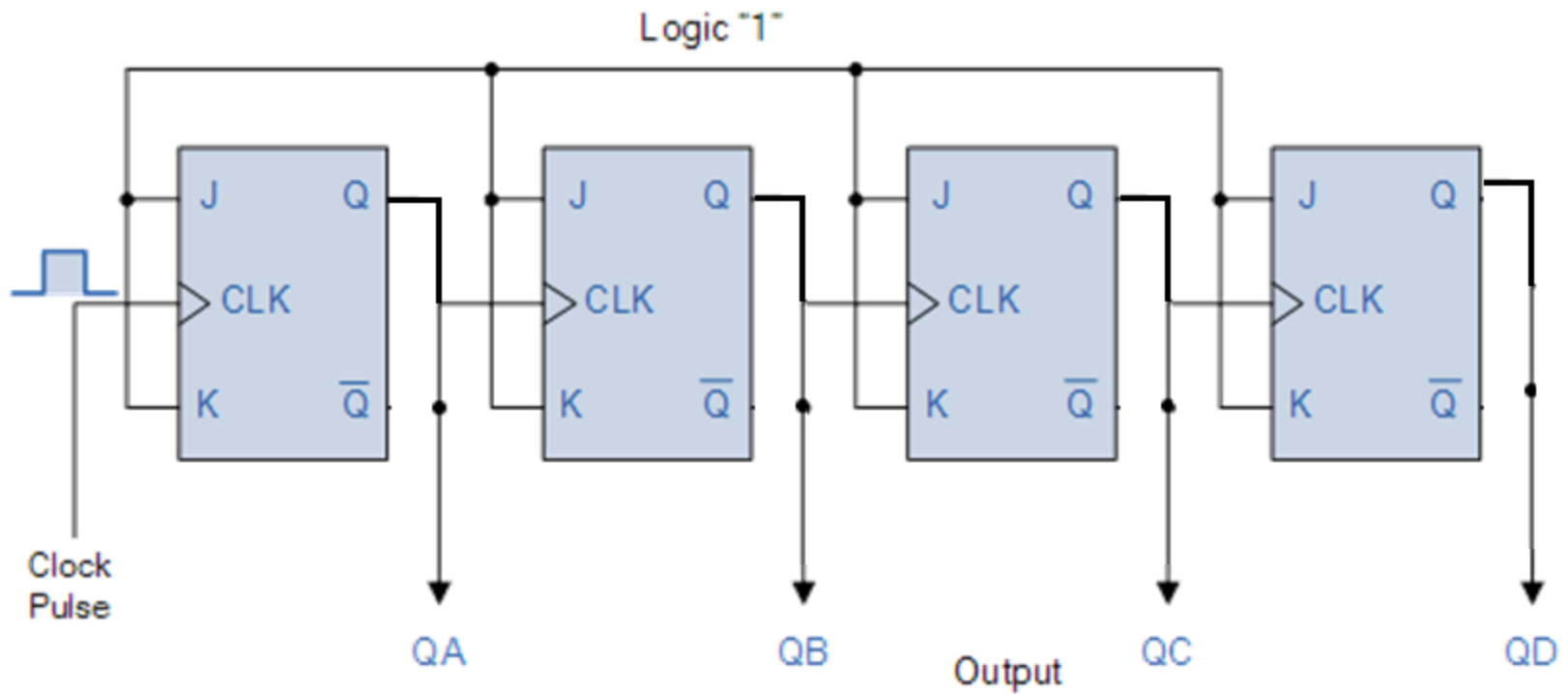


COUNTERS

4-BIT ASYNC. UP COUNTER

 

COUNTERS

4-BIT ASYNC. DOWN COUNTER

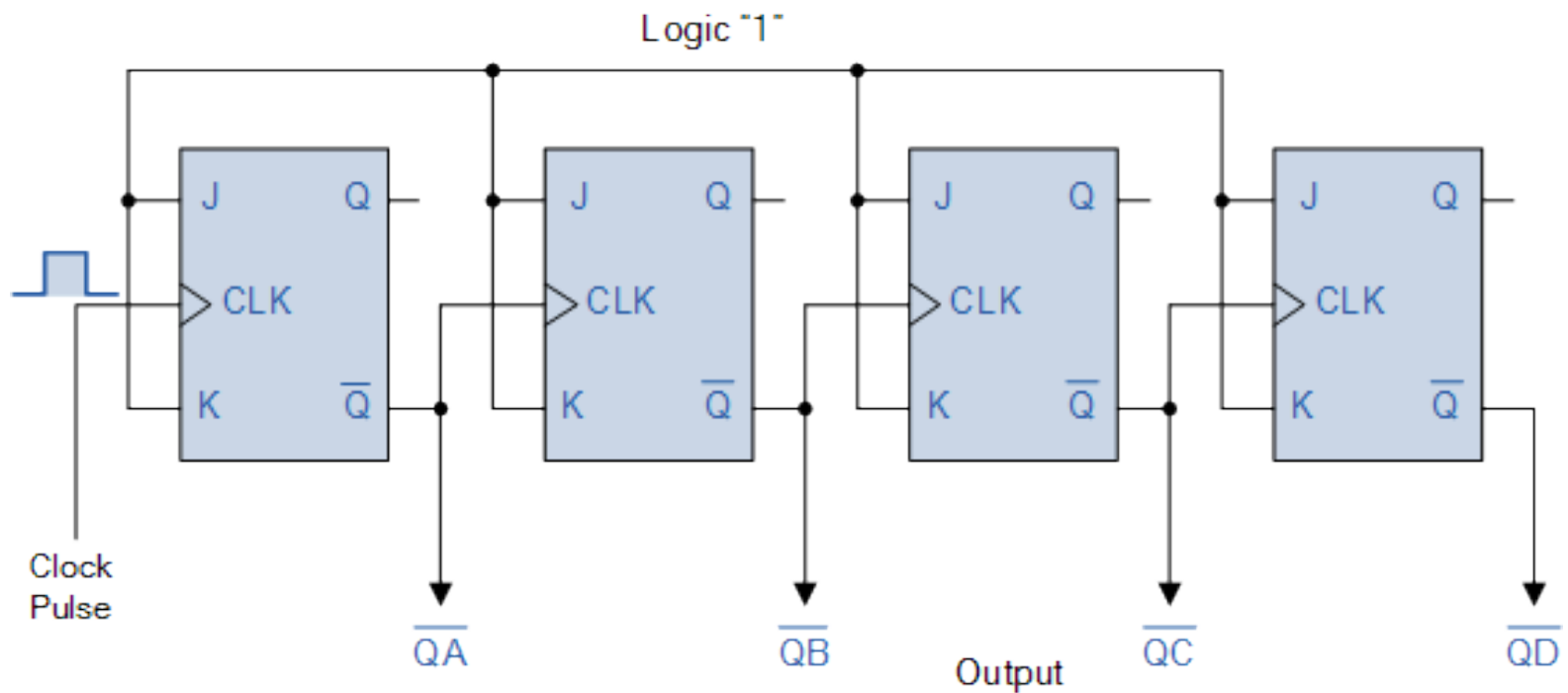

COUNTERS

SYNC. MOD COUNTER DESIGN

- ❑ The counter can be designed using any types of Flip flop. But in general T-Flip flop is used to design counter.
- ❑ The use of MOD counter in to counter value for specific number of times.
- ❑ For example, MOD-5 Counter means it can counter the values from 0 to 4 and it get reset. So, it count in the sequence of 000,001,0110,011,100,000,001,etc.,
- ❑ The number of flip flop required to design MOD counter is depends on the number of count it performs.

COUNTERS

SYNC. MOD COUNTER DESIGN

1. Determine the number of Flip-Flop needed
2. Choose the type of Flip Flop and its excitation table
3. Determine Transition table
4. K-Map simplification procedures for driving expressions
5. Draw the logic diagram

COUNTERS

Example:1 Design of MOD-6 Counter using JK Flip flop

Step 1 : Find number of flip-flops required to build the counter.

Flip-flops required are : $2^n \geq N$

Here $N = 6 \quad \therefore n = 3$

i.e. Three flip-flops are required.

Step 2 : Write an excitation table for JK flip-flop.

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

COUNTERS

Example:1 Design of MOD-6 Counter using JK Flip flop

Step 3 : Determine the transition table.

[illegible]

COUNTERS

Example:1 Design of MOD-6 Counter using JK Flip flop

Step 4 : K-map simplification for flip-flop inputs.

For J_A

$Q_B Q_C$	00	01	11	10
Q_A 0	0	0	1	0
Q_A 1	X	X	X	X

$$J_A = Q_B Q_C$$

For K_A

$Q_B Q_C$	00	01	11	10
Q_A 0	X	X	X	X
Q_A 1	0	1	X	X

$$K_A = Q_C$$

For J_B

$Q_B Q_C$	00	01	11	10
Q_A 0	0	1	X	X
Q_A 1	0	0	X	X

$$J_B = \bar{Q}_A Q_C$$

For K_B

$Q_B Q_C$	00	01	11	10
Q_A 0	X	X	1	0
Q_A 1	X	X	X	X

$$K_B = Q_C$$

For J_C

$Q_B Q_C$	00	01	11	10
Q_A 0	1	X	X	1
Q_A 1	1	X	X	X

$$J_C = 1$$

For K_C


$Q_B Q_C$	00	01	11	10
Q_A 0	X	1	1	X
Q_A 1	X	1	X	X

$$K_C = 1$$

COUNTERS

Example:1 Design of MOD-6 Counter using JK Flip flop

Step 5 : Implement the counter.

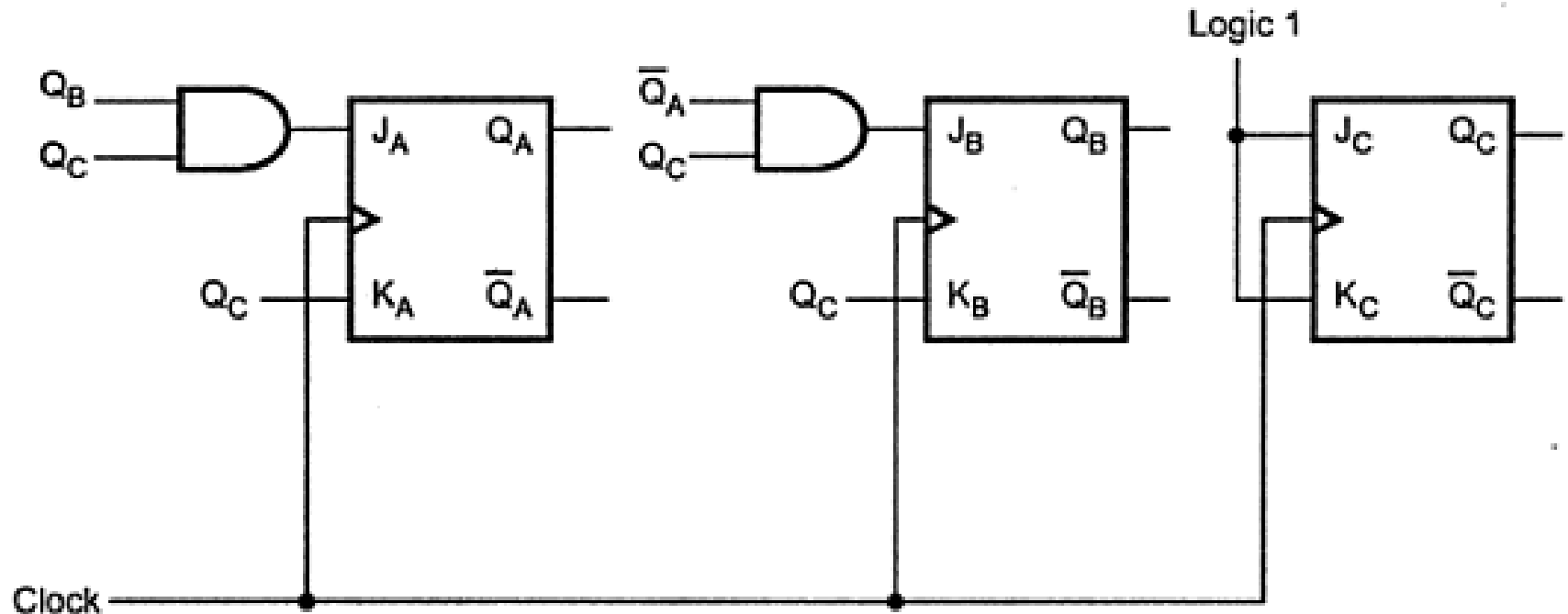

COUNTERS

Example:2 Design of MOD-6 Counter using T Flip flop

Step 1 : Find number of flip-flops required to build the counter.

Flip-flops required are : $2^n \geq N$

Here $N = 6 \therefore n = 3$

i.e. Three flip-flops are required.

Step 2 : Write an excitation table for T flip-flop.

Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

COUNTERS

Example:2 Design of MOD-6 Counter using T Flip flop

Step 3 : Determine the transition table.

Present state			Next state			Flip-flop inputs		
Q_A	Q_B	Q_C	Q_{A+1}	Q_{B+1}	Q_{C+1}	T_A	T_B	T_C
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	0	0	0	1	0	1
1	1	0	x	x	x	x	x	x
1	1	1	x	x	x	x	x	x

COUNTERS

Example:2 Design of MOD-6 Counter using T Flip flop

Step 4 : K-map simplification for flip-flop inputs.


 



Fig. 8.82

Step 5 : Implement the counter.

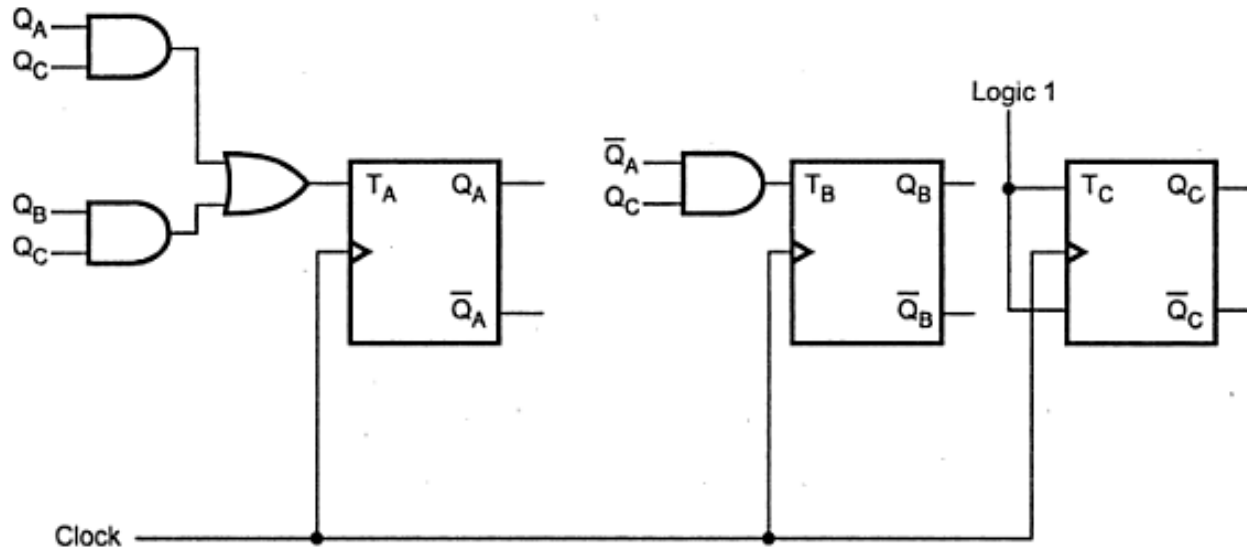

COUNTERS

JOHNSON COUNTERS

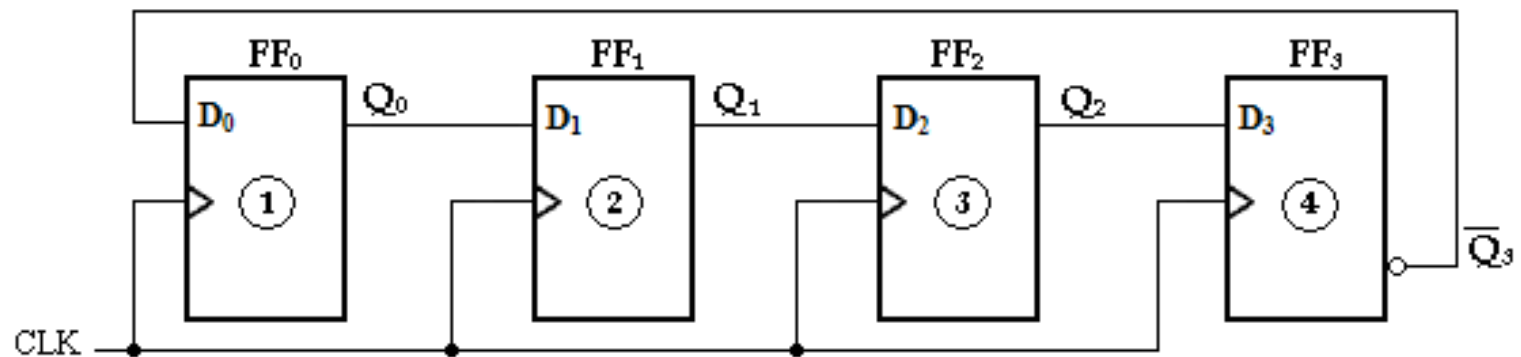

4-Bit Johnson Counter


COUNTERS

JOHNSON COUNTERS

Clock Input	Q3	Q2	Q1	Q0
1	0	0	0	0
2	0	0	0	1
3	0	0	1	1
4	0	1	1	1
5	1	1	1	1
6	1	1	1	0
7	1	1	0	0
8	1	0	0	0

COUNTERS


JOHNSON COUNTERS

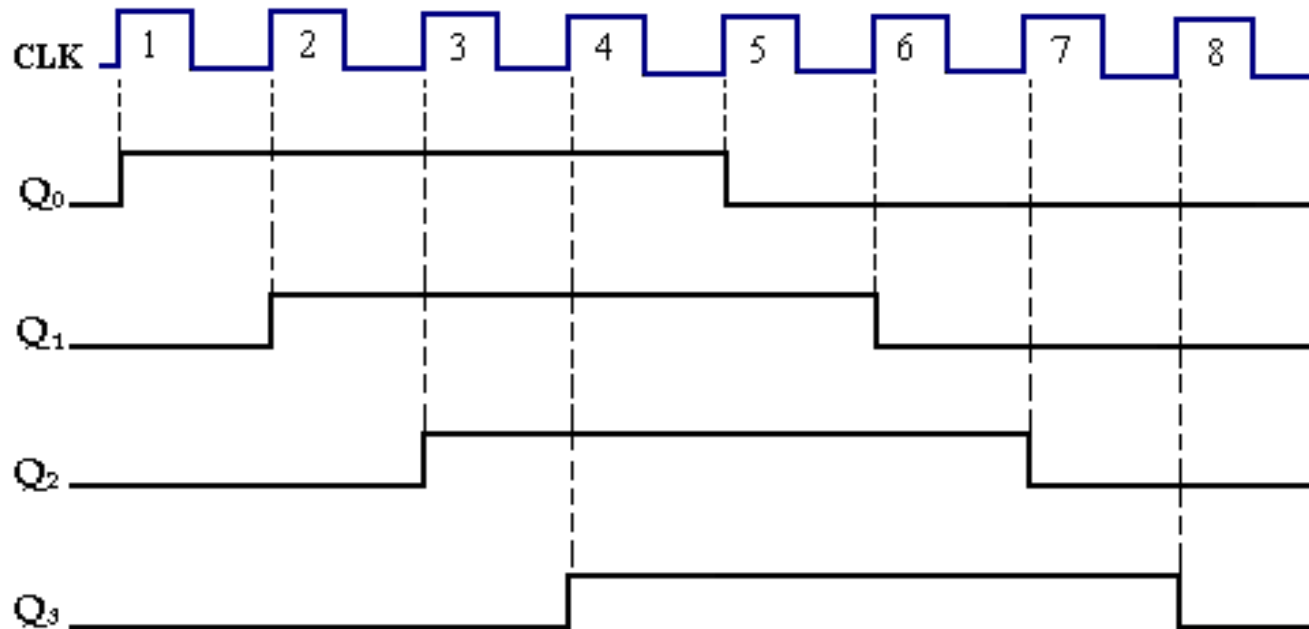

Time sequence for a 4-bit Johnson counter

COUNTERS

RING COUNTERS

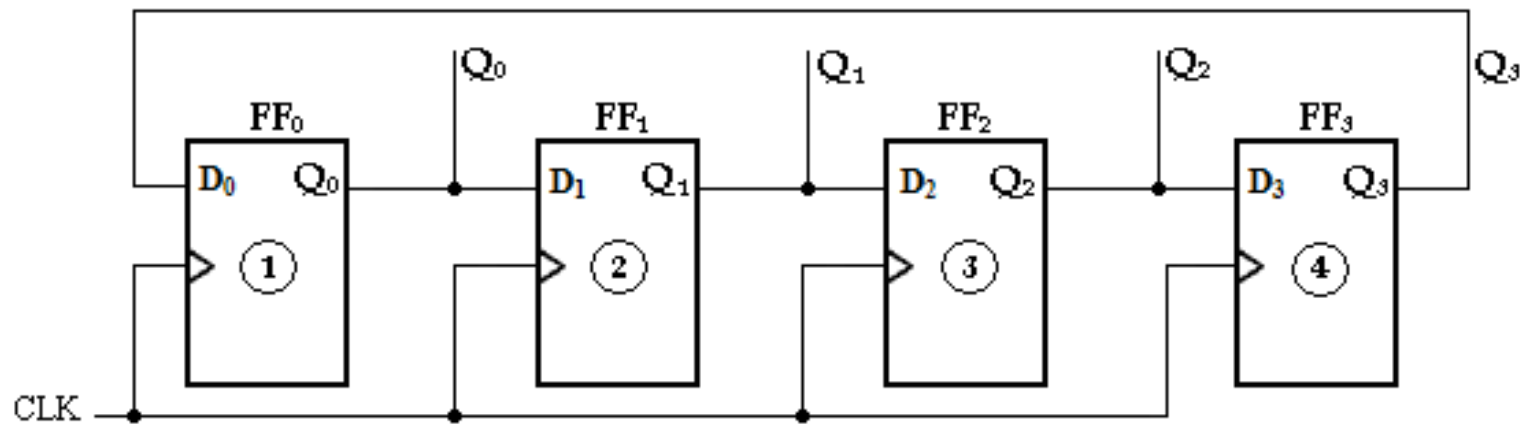

Ring counter


COUNTERS

RING COUNTERS

Clock Input	Q3	Q2	Q1	Q0
1	0	0	0	1
2	0	0	1	0
3	0	1	0	0
4	1	0	0	0
5	0	0	0	1
6	0	0	1	0
7	0	1	0	0
8	1	0	0	0

COUNTERS

RING COUNTERS

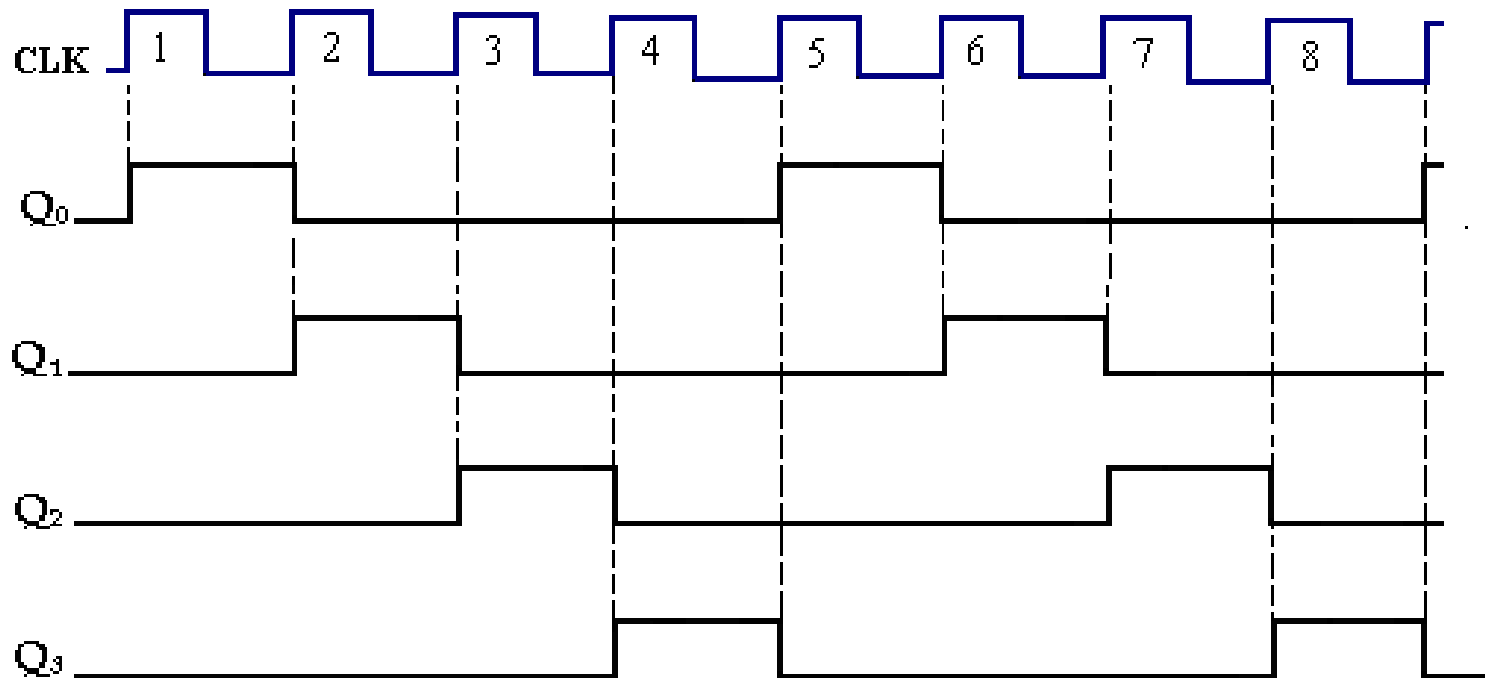

Time sequence for a Ring counter

COUNTERS

```
module upordown_counter( Clk,  reset,  UpOrDown,  Count );
  input Clk,reset,UpOrDown;
  output [3 : 0] Count;
  reg [3 : 0] Count = 0;
  always @(posedge(Clk) or posedge(reset))
  begin
    if(reset == 1)
      Count <= 0;
    else
      if(UpOrDown == 1) //Up mode selected
        if(Count == 15)
          Count <= 0;
        else
          Count <= Count + 1; //Increment Counter
      else //Down mode selected
        if(Count == 0)
          Count <= 15;
        else
          Count <= Count - 1; //Decrement counter
    end
  endmodule
```

COUNTERS

Example: Mod N Counter

```
// # (parameter N = 10, parameter WIDTH = 4)
```

```
module modN_ctr ( input  clk, input  rstn, output reg[WIDTH-1:0] out);
```

```
    always @ (posedge clk) begin
```

```
        if (!rstn) begin
```

```
            out <= 0;
```

```
        end else begin
```

```
            if (out == N-1)
```

```
                out <= 0;
```

```
            else
```

```
                out <= out + 1;
```

```
        end
```

```
    end
```

```
endmodule
```

COUNTERS

```
module tb;
  parameter N = 10;
  parameter WIDTH = 4;
  reg clk;
  reg rstn;
  wire [WIDTH-1:0] out;

  modN_ctr u0 ( .clk(clk), .rstn(rstn), .out(out));

  always #10 clk = ~clk;

  initial begin
    {clk, rstn} <= 0;
    repeat(2) @ (posedge clk);
    rstn <= 1;
    repeat(20) @ (posedge clk);
    $finish;
  end
endmodule
```