

Additional Practice Problems- Set 2

(To be submitted on 14.10.2022 at 11 am)

1. Implement the function $\sum m(1,3,4,11,12,13,14,15)$ using an 8:1 mux.
2. Implement the function $\sum m(1,3,5,7,11,13,15)$ using a suitable demux
3. Design an odd parity generator using logic gates
4. Write the Verilog code for odd parity generator (with test bench) using data flow modelling