

Module 1 Digital Logics

Lec 1.5 Review of Logic families

Review of CMOS & TTL logic families

REVIEW OF LOGIC GATE FAMILIES

INTRODUCTION

- ❑ In Digital Electronics, a logic family refers to digital integrated circuit devices which are constructed with a combination of electronic gates.
- ❑ There are different families of logic gates. Each family has its own characteristics, limitations and advantages.
- ❑ Some families also have common characteristics. Also within each family, there is a range of voltages which may be high level or low level.

REVIEW OF LOGIC GATE FAMILIES

INTRODUCTION

□ These families are listed below:

- Diode Logic (DL)
- Resistor-Transistor Logic (RTL)
- Diode-Transistor Logic (DTL)
- Emitter Coupled Logic (ECL)
- Transistor-Transistor Logic (TTL) ✓
- Complementary Metal Oxide Semiconductor Logic (CMOS) ✓

REVIEW OF LOGIC GATE FAMILIES


CMOS LOGIC

- ❑ CMOS is known for its low power consumption and high fan-out. It is also considered to be one of the most reliable logic family today.
- ❑ The transistors inside the CMOS are made from an NMOS transistor and PMOS transistor.
- ❑ To realize the logical functions, both P-type and N-type transistors are used. It is currently being used in microprocessor technology and Application Specific Integrated Circuits(ASIC).

REVIEW OF LOGIC GATE FAMILIES

CMOS LOGIC

 - ❑ The gate of a MOS transistor controls the flow of the current between the drain and the source
- ❑ The MOS transistor can be viewed as a simple ON/OFF switch




REVIEW OF LOGIC GATE FAMILIES

CMOS LOGIC - inverter


- ❑ CMOS gates are built around the technology of the basic CMOS inverter
- ❑ Two Transistors are enhancement mode MOSFETs and Transistors come in complementary pairs
- ❑ N-Channel with its source grounded & P-Channel with its source connected to +V
- ❑ Input: gates connected together & Output: drains connected

REVIEW OF LOGIC GATE FAMILIES

CMOS LOGIC - inverter

 


| in | p1 | n1 | out |
|----|-----|-----|-----|
| 0 | ON | OFF | 1 |
| 1 | OFF | ON | 0 |

 

REVIEW OF LOGIC GATE FAMILIES

CMOS LOGIC - NAND

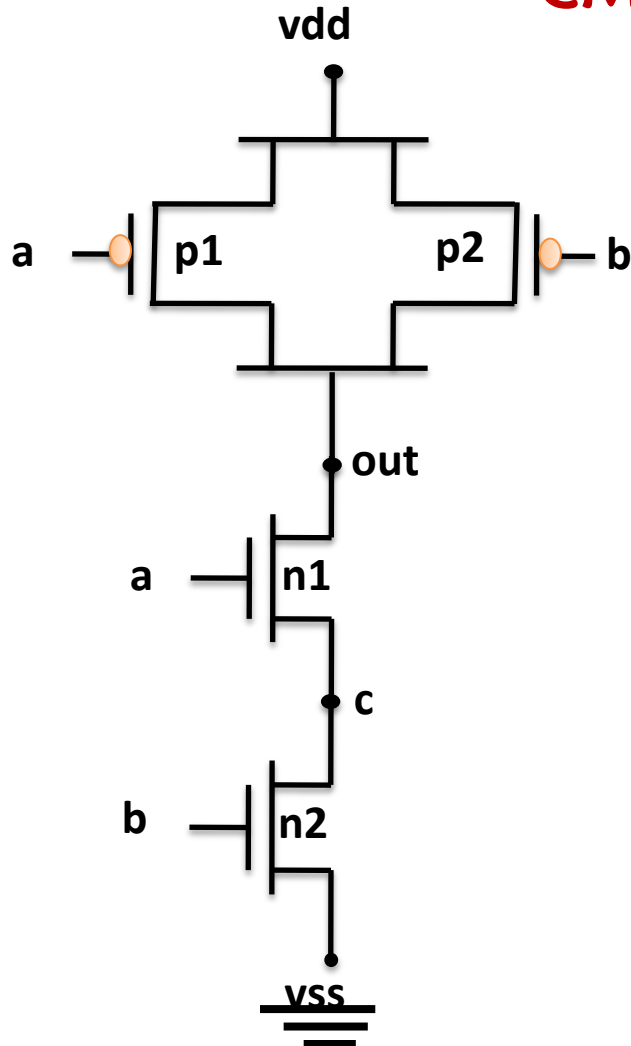


| a | b | p1 | p2 | n1 | n2 | out |
|---|---|-----|-----|-----|-----|-----|
| 0 | 0 | ON | ON | OFF | OFF | 1 |
| 0 | 1 | ON | OFF | OFF | ON | 1 |
| 1 | 0 | OFF | ON | ON | OFF | 1 |
| 1 | 1 | OFF | OFF | ON | ON | 0 |

REVIEW OF LOGIC GATE FAMILIES


CMOS LOGIC - NOR

| a | b | p1 | p2 | n1 | n2 | out |
|---|---|-----|-----|-----|-----|-----|
| 0 | 0 | ON | ON | OFF | OFF | 1 |
| 0 | 1 | ON | OFF | OFF | ON | 0 |
| 1 | 0 | OFF | ON | ON | OFF | 0 |
| 1 | 1 | OFF | OFF | ON | ON | 0 |

 

REVIEW OF LOGIC GATE FAMILIES

CMOS LOGIC - EXAMPLES

 


4 INPUT


CMOS NOR GATE

REVIEW OF LOGIC GATE FAMILIES

CMOS LOGIC - AND

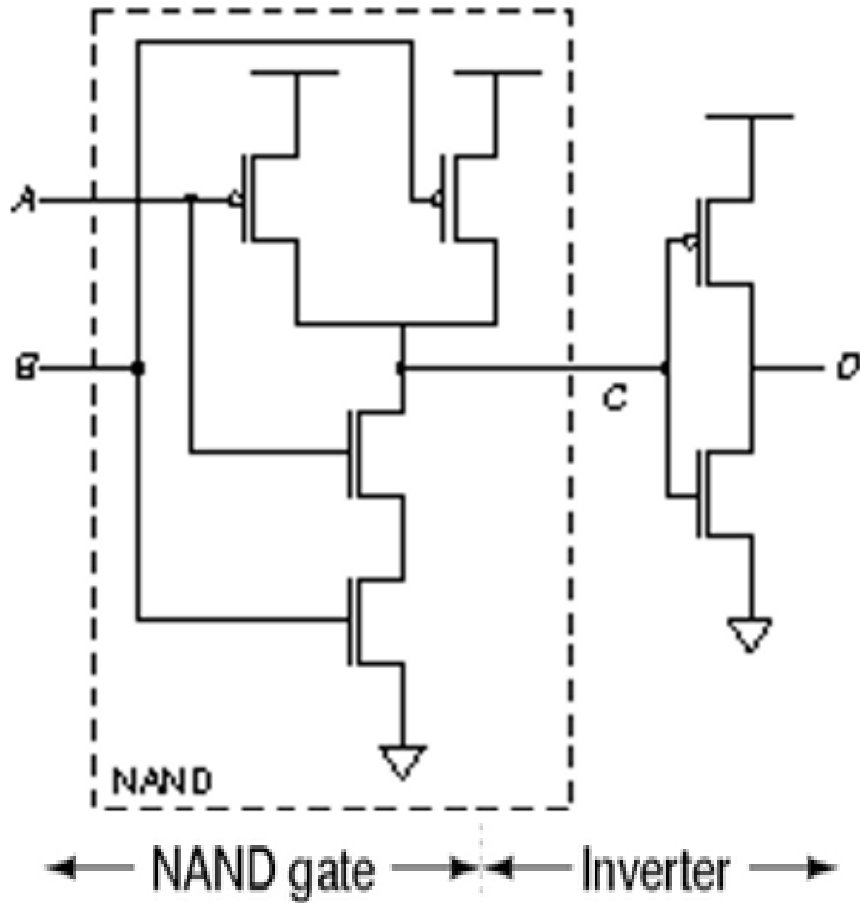


CMOS LOGIC - OR

 

REVIEW OF LOGIC GATE FAMILIES

CMOS LOGIC - EXAMPLES

$$Y = \overline{(A + B + C)} \cdot D$$

 


REVIEW OF LOGIC GATE FAMILIES

CMOS LOGIC - EXAMPLES

How to implement

$$F = ab + bc + ca$$

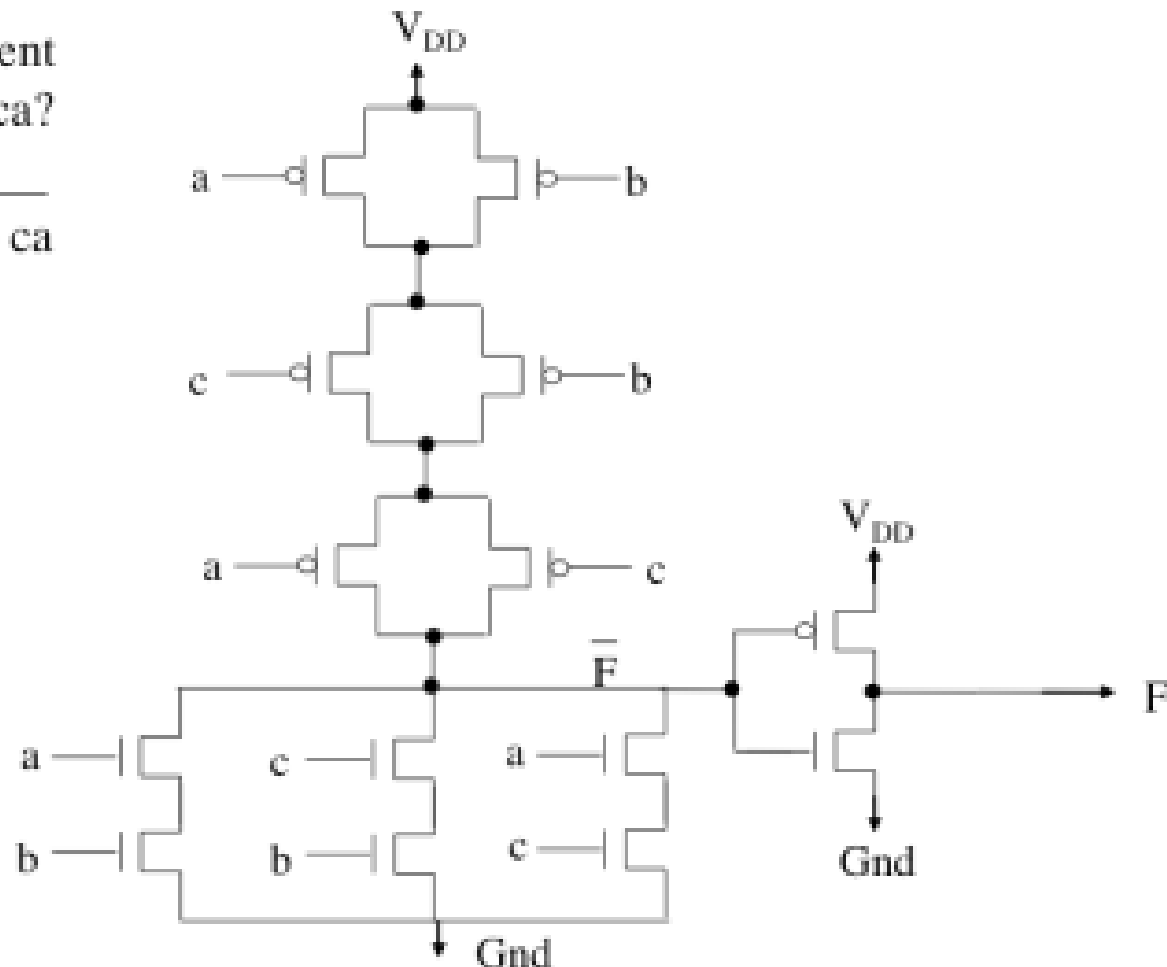• $\overline{F} = \overline{ab + bc + ca}$



REVIEW OF LOGIC GATE FAMILIES

EXERCISE PROBLEMS

Realize following logical expressions using CMOS logic:

1. $Y = (AB+C)'$
2. $Y = AB' + A'B$
3. $Y = B'C + ABC'$
4. $Y = (A(BC+D))'$
5. $Y = (AB + A(C+D))'$
6. $Y = (ABC + DE + F)$

REVIEW OF LOGIC GATE FAMILIES

TRANSISTOR-TRANSISTOR LOGIC (TTL)


- ❑ TTL has become the standard logic circuit in many application for a number of years.
- ❑ TTL greatly decreases the manufacturing costs because multiple emitters can be added in the input so no extra space is needed and a multiple input gate can be constructed easily.
- ❑ A commercial IC package of TTL includes three three-input gates, four two-input gates, or two four-input gates. The structure of the IC always remains the same.

REVIEW OF LOGIC GATE FAMILIES

TRANSISTOR-TRANSISTOR LOGIC (TTL)

- ❑ In transistor-transistor logic, the logic gates are constructed around the transistors.
- ❑ TTL uses bipolar transistors to construct its integrated circuits.
- ❑ There have been different versions of TTL:
 - Standard TTL.
 - High speed TTL.
 - Low power TTL.
 - Schottky TTL.

TTL- Transistor Transistor Logic

 


CASE 1:

- **INPUT :LOW**
 - corresponding base-emitter junction is forward biased and the base-collector junction is reverse biased.
 - transistor Q2 is cut off and also transistor Q4 is cut off
 - Transistor Q3 goes to saturation and diode D2 starts conducting and output is connected to V_{CC} and goes to logic high
- INPUT:high


TRANSISTOR-TRANSISTOR LOGIC (TTL)

TTL NAND Gate

 

LOW = 0V

HIGH = 5V

 

| V_1 | V_2 | State of Q1 | State of Q2 | State of Q3 | V_{out} |
|-------|-------|-------------|-------------|-------------|-----------|
| LOW | LOW | ON | OFF | OFF | HIGH |
| LOW | HIGH | ON | OFF | OFF | HIGH |
| HIGH | LOW | ON | OFF | OFF | HIGH |
| HIGH | HIGH | OFF | ON | ON | LOW |

Case 1:

Any i/p is logic 0

Q1 : BE-Forward Bias

BC- Reverse Bias

So Q2 and Q3 are off

$V_{out} = V_{cc} - I_c R_c$ logic 1

Case 2:

Any i/p is are 1

Q1 : BE-Reverse Bias

BC- Forward Bias

So Q2 and Q3 are ON

$V_{out} = V_{cc} - I_c R_c$ 0.2 volts Logic 0

REVIEW OF LOGIC GATE FAMILIES

SUMMARY

| <i>Logic Parameters</i> | <i>RTL</i> | <i>DTL</i> | <i>TTL</i> | <i>ECL</i> | <i>CMOS</i> |
|--|------------|----------------|--------------|------------|----------------------------|
| Basic gates with +ve logic | NOR | NAND | NAND | OR/NOR | NAND/NOR |
| Maximum fan-in | 5 | 10 | 8 | 5 | 8 |
| Fan out | 5 | 8 | 10 | 25 | >50 |
| Power dissipation/ gate (in mW) | 12 | 10 | 10 | 50 | 0.01 static at 1 MHz |
| Propagation delay per gate (nano sec) | 20 | 30 | 12 | 4 | 70 |
| Noise Immunity | Nominal | Good | Very good | Good | Very good |
| Number of functions | High | Fairly high | Very high | High | Good |
| Clock rate, MHz | 5 | 12 | 15 | 300 | 5 |

END