



Final Assessment Test (FAT) - JUNE/JULY 2023

Programme	B.Tech.	Semester	Winter Semester 2022-23
Course Title	DIGITAL SYSTEMS DESIGN	Course Code	BECE102L
Faculty Name	Prof. Mohamed Imran A	Slot	B1+TB1
		Class Nbr	CH2022232300550
Time	3 Hours	Max. Marks	100


Section I (7 X 10 Marks)
Answer All questions

01. For the given Boolean function, [10]

$$F(W, X, Y, Z) = X\bar{Y}Z + \bar{X}\bar{Y}Z + \bar{W}XY + W\bar{X}Y + WXY$$


- Obtain the truth table of F and represent the function with minterms.
 - Use Boolean algebra to simplify the function and realize the circuit using NAND gates.
 - Write a Verilog code to implement the function using structural modelling.
02. Design a combinational circuit to generate EVEN parity and ODD parity. Write the truth table with $(ABCD)$ as inputs and X (Even), Y (Odd) as outputs. [10]
- Implement the output X using 4×1 multiplexer.
 - Implement the output Y using 3×8 decoder.

 03. Comprehend the circuit shown below and find the outputs $(S_3S_2S_1S_0)$, C and V for $M = 0$ and $M = 1$. Assume $A = +6$ and $B = +4$. What does V indicate? Validate your answer with the calculations. [10]



04. (a) The sequence 1011 is applied to the input of a 4-bit shift register(SISO) that is initially cleared. What is the state of the shift register after three clock pulses? Explain with timing diagram/table. [10]

 
- (b) Draw the output states of each flipflop for the data signal given below



05. Design and draw the state diagram of a FSM to detect two sequences 1010 and 110 for the following cases: [10]

- Mealy model with overlapping states
- Moore model with non overlapping states.

 06. Design an modulo 8 asynchronous counter using negative edge triggered JK Flip Flop [10]
 (a) the counter should count with a truncated sequence 2,3,4,5,6.
 (b) draw the timing diagram and verify the output.
07. Derive the state table and the state diagram of the sequential circuit shown below, where x is the [10]
 input and y is the output.



Section II (2 X 15 Marks)

Answer ALL questions

08. The arithmetic operation $C = A * B$ is performed on a digital system. [15]
 (a) Tabulate the calculation steps using Booth Algorithm, if $A = +5$ and $B = -4$
 (b) Write the Verilog code for implementing the same operation with Array Multiplier using dataflow modelling.
09. Implement the combinational circuit [15]
 $F1(W, X, Y, Z) = \sum(2, 12, 13).$
 $F2(W, X, Y, Z) = \sum(7, 8, 9, 10, 11, 12, 13, 14, 15),$
 $F3(W, X, Y, Z) = \sum(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15),$
 $F4(W, X, Y, Z) = \sum(1, 2, 8, 12, 13)$
 (a) using Programmable Logic Array (PLA).
 (b) using Programmable Array Logic (PAL).

