


# **MODULE - 7**

# Programmable Logic Devices

---

- General purpose chip for implementing circuits
- Can be customized using programmable switches
- Main types of PLDs
  - PLA
  - PAL
  - CPLD
  - FPGA

# Programmable Logic Devices

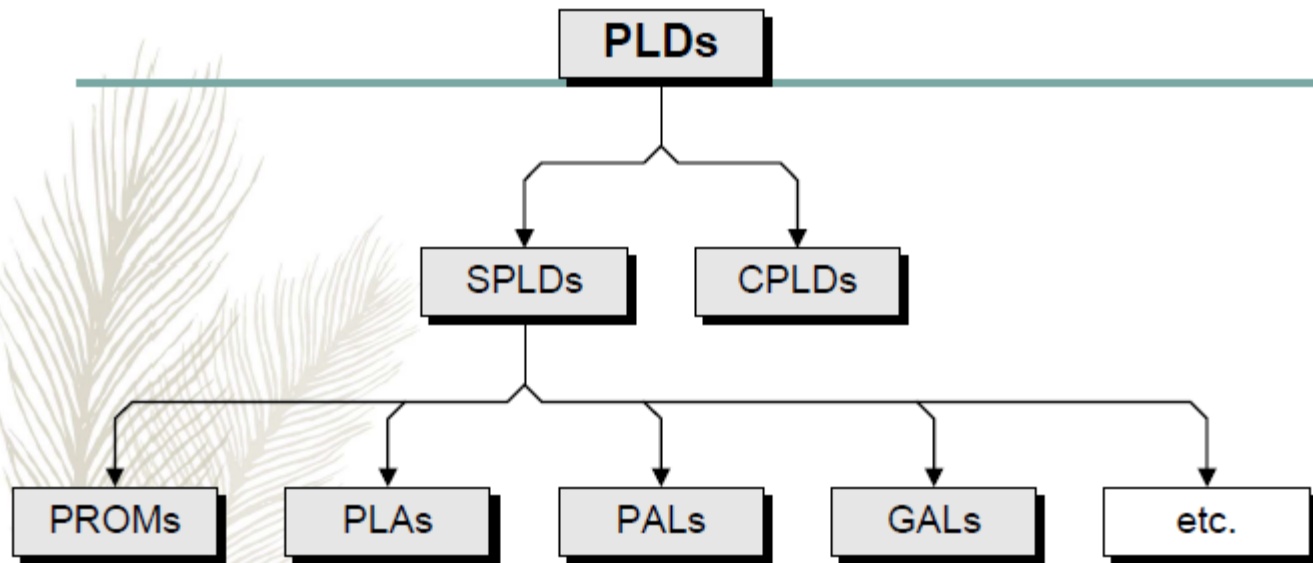


# Programmable Logic Devices

---

- The purpose of a PLD device is to permit elaborate digital logic designs to be implemented by the user in a single device.
- Can be erased electrically and reprogrammed with a new design, making them very well suited for academic and prototyping
- Types of Programmable Logic Devices
- SPLDs (Simple Programmable Logic Devices)
  - ROM (Read-Only Memory)
  - PLA (Programmable Logic Array)
  - PAL (Programmable Array Logic)
  - GAL (Generic Array Logic)
- CPLD (Complex Programmable Logic Device)
- FPGA (Field-Programmable Gate Array)

# General structure of PLDs

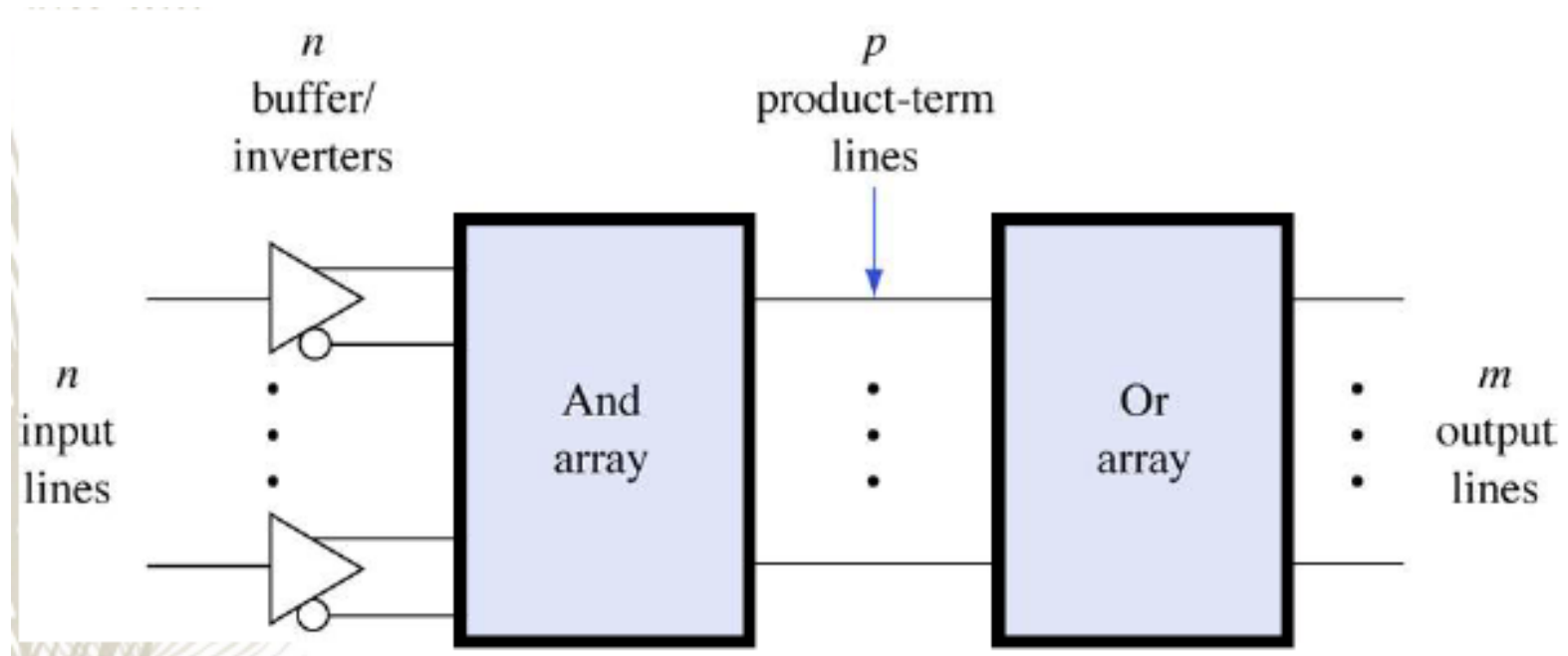

# General structure of PLDs

The differences between the first three categories are these:

- In a ROM, the input connection matrix is hardwired. The user can modify the output connection matrix.
- In a PAL/GAL the output connection matrix is hardwired. The user can modify the input connection matrix.
- In a PLA the user can modify both the input connection matrix and the output connection matrix.

Device	AND-array	OR-array
PROM	Fixed	Programmable
PLA	Programmable	Programmable
PAL	Programmable	Fixed
GAL	Programmable	Fixed

# Programming by blowing fuses




(a) Before programming.

OR - PLD Notation




(b) After programming.


AND - PLD Notation

 


OR gate before programming

 

AND gate before programming

 


OR gate after programming

 


AND gate after programming

# Programming by blowing fuses

 




# Gate Level Version of PLA

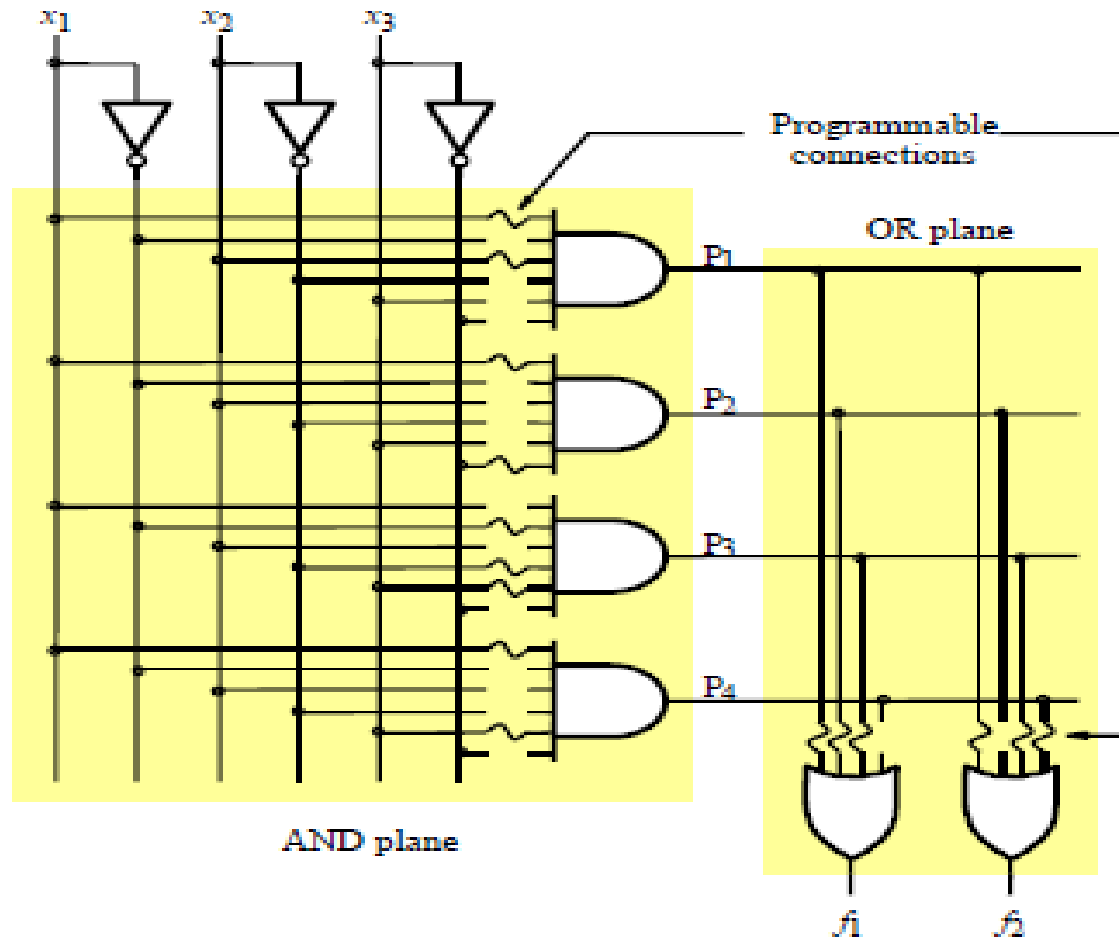

 
# Function Implementation in PLA

$$f_1 = x_1x_2 + x_1x_3' + x_1'x_2'x_3 \text{ \& } f_2 = x_1x_2 + x_1'x_2'x_3 + x_1x_3$$



# Example

- $A = XY + XZ'$
- $B = XY' + YZ + XZ'$

 

## Ex2

- $F1 = AB' + AC + A'BC'$
- $F2 = (AC + BC)'$

## Ex3

- $F1(A,B,C)=\sum(0,1,2,4)$
- $F2(A,B,C)=\sum(0,5,6,7)$

## Ex4

- $F = \sum(1,2,4,5,7)$  USING pla
- Ex5
- $F = \sum(0,1,3,5,7)$

## Ex6

- $F = \sum m(0, 2, 6, 7, 8, 9, 12, 13, 14)$

# Design for PLA

---

Implement the following functions using PLA


$$F0 = A + B' C'$$

$$F1 = A C' + A B$$

$$F2 = B' C' + A B$$

$$F3 = B' C + A$$



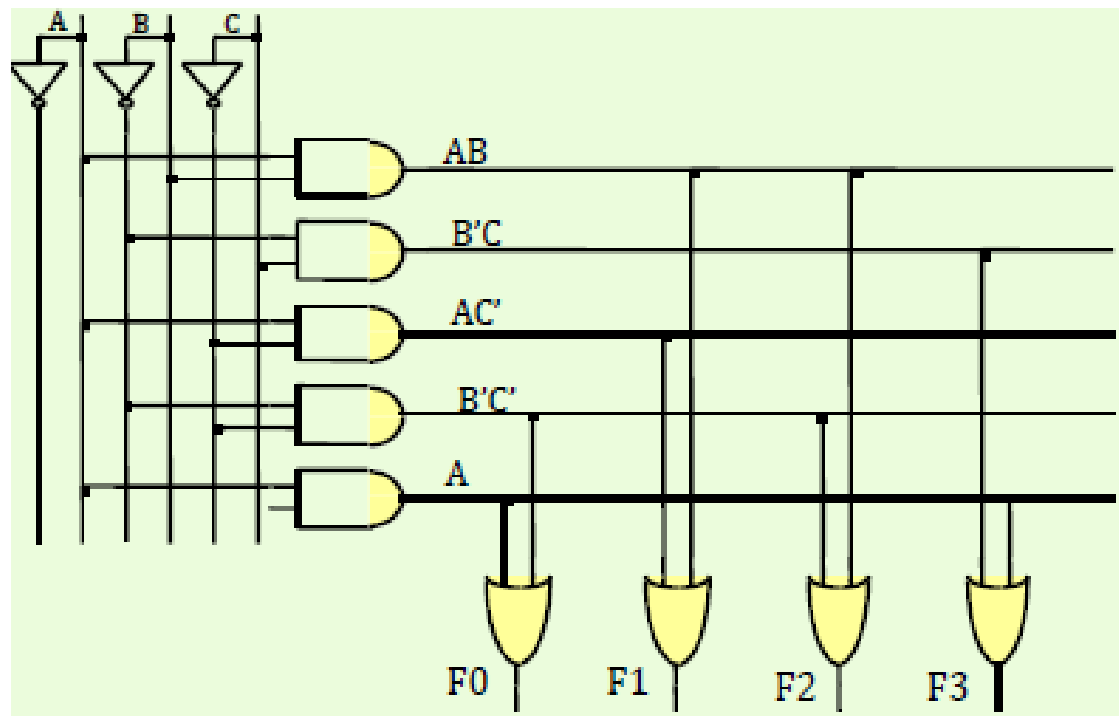

# Design for PLA


Implement the following functions using PLA

$$W = A + B D + B C$$

$$X = B C'$$


$$Y = B + C$$

$$Z = A'B'C'D + B C D + A D' + B' C D'$$

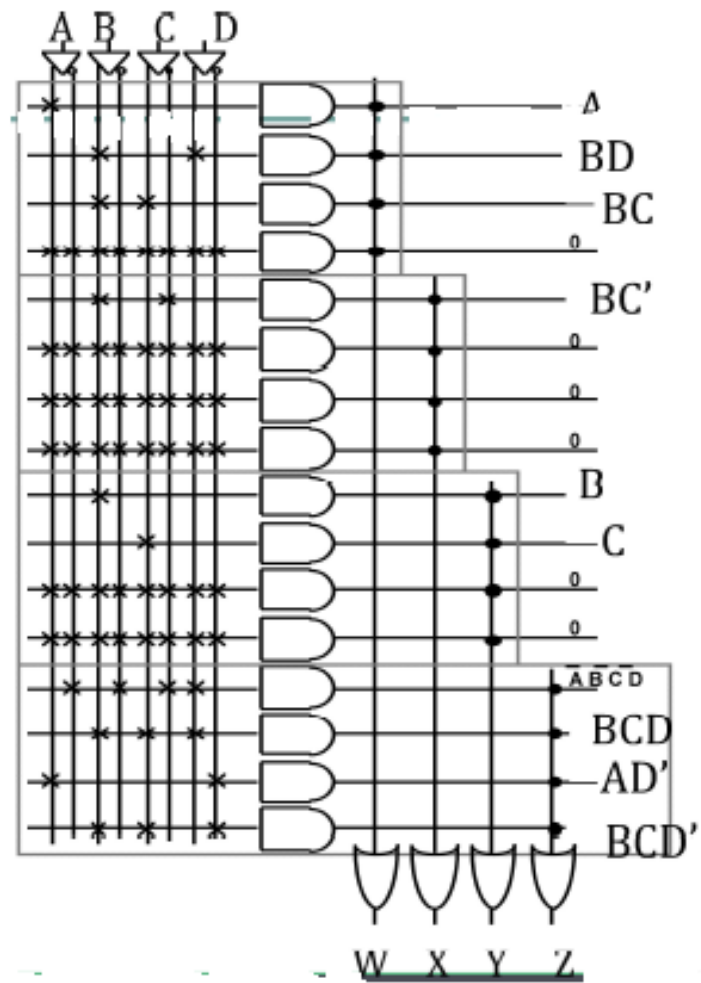
 
# Programmable Array Logic (PAL)

- Also used to implement circuits in SOP form
- The connections in the AND plane are programmable
- The connections in the OR plane are NOT programmable




# Programmable Array Logic (PAL)

Implement the following functions in PAL

$$f_1 = x_1x_2x_3' + x_1'x_2x_3$$

$$f_2 = x_1'x_2' + x_1x_2x_3$$

 


# Programmable Array Logic (PAL)

Implement the following functions in PAL

$$W = AB'C + CD$$

$$X = A'BC + A'CD + ACD + BCD$$

$$Y = A'CD + ACD + A'BD$$

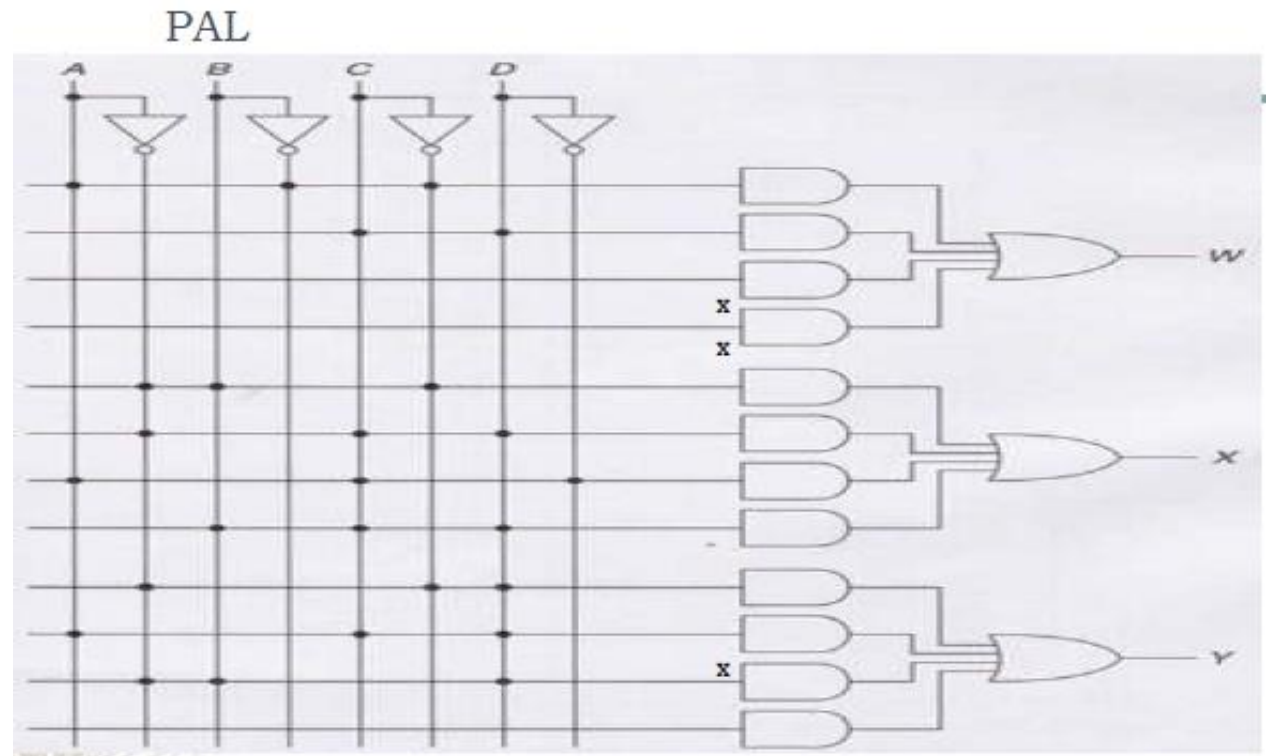

## Comparison of PALs and PLAs

---

- PALs have the same limitations as PLAs (small number of allowed AND terms) plus they have a fixed OR plane less flexibility than PLAs
- PALs are simpler to manufacture, cheaper, and faster (better performance)
- PALs also often have extra circuitry connected to the output of each OR gate

# Ex

- $W(A,B,C,D)=\sum m(2,12,13)$
- $X(A,B,C,D)=\sum m(7,8,9,10,11,12,13,14,15)$
- $Y(A,B,C,D)=\sum m(0,2,3,4,5,6,7,8,10,11,15)$
- $Z(A,B,C,D)=\sum (1,2,8,12,13)$



## Ex4

- $F = \sum(1, 2, 4, 5, 7)$
- $F = \sum(0, 1, 3, 5, 7)$

## Ex5

- $F = \sum m(0, 2, 6, 7, 8, 9, 12, 13, 14)$


## FPGA AND CPLD

- FPGA - Field-Programmable Gate Array.
- CPLD - Complex Programmable Logic Device
- FPGA and CPLD is an advance PLD.
- Support thousands of gate where as PLD only support hundreds of gates.

# CPLD

- CPLDs contain multiple circuit blocks on a single chip
- Each block is like a PAL: PAL-like block
- Connections are provided between PAL-like blocks via an interconnection network that is programmable
- Each block is connected to an I/O block as well

# Structure of a CPLD

 

# FPGA


- SPLDs and CPLDs are relatively small and useful for simple logic devices Up to about 20000 gates
- Field Programmable Gate Arrays (FPGA) can handle larger circuits
- No AND/OR planes
- Provide logic blocks, I/O blocks, and interconnection wires and switches
- Logic blocks provide functionality
- Interconnection switches allow logic blocks to be connected to each other and to the I/O pins




- CLB consists of a
  - programmable lookup table
  - multiplexers
  - registers
  - paths for control signals



# 6T SRAM cell

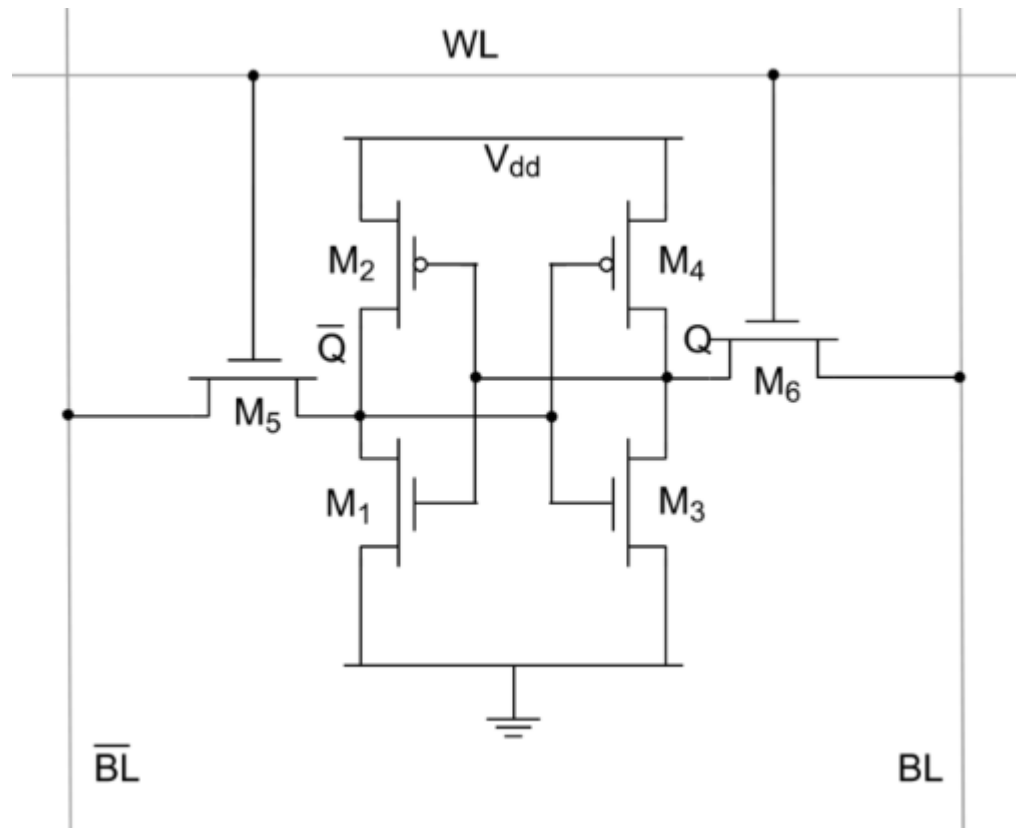

# LUTs

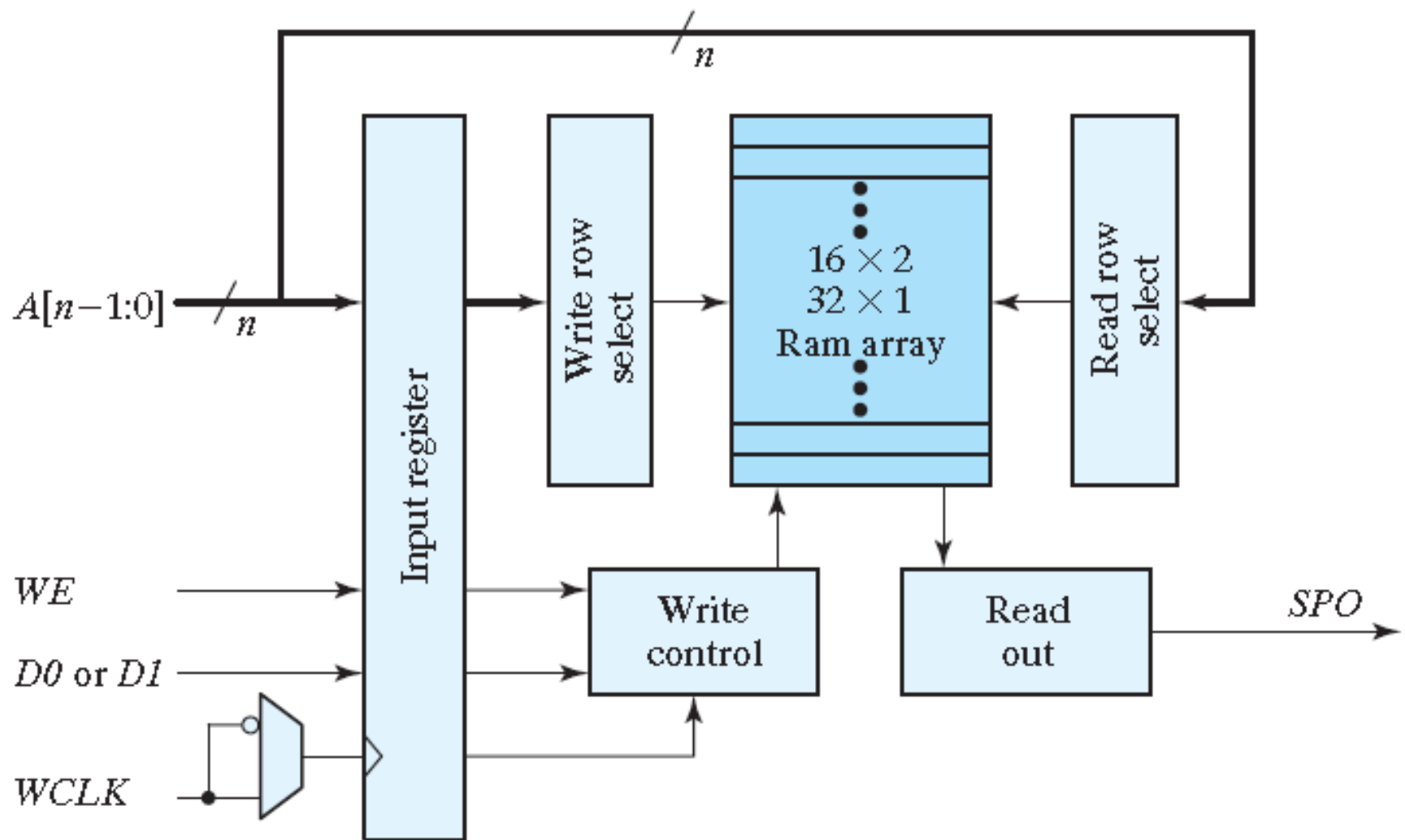


# Xilinx Spartan-3E Starter Kit


FPGA

buttons

LEDs

switches

 

 


Leaf Cells (6)

- a\_IBUF\_inst (IBUF)
- b\_IBUF\_inst (IBUF)
- cout\_OBUF\_inst (OBUF
- cout\_OBUF\_inst\_i\_1 (L
- sum\_OBUF\_inst (OBU
- sum\_OBUF\_inst\_i\_1 (L

Cell Prop

sum\_OBUF\_inst

Name: sum\_OI

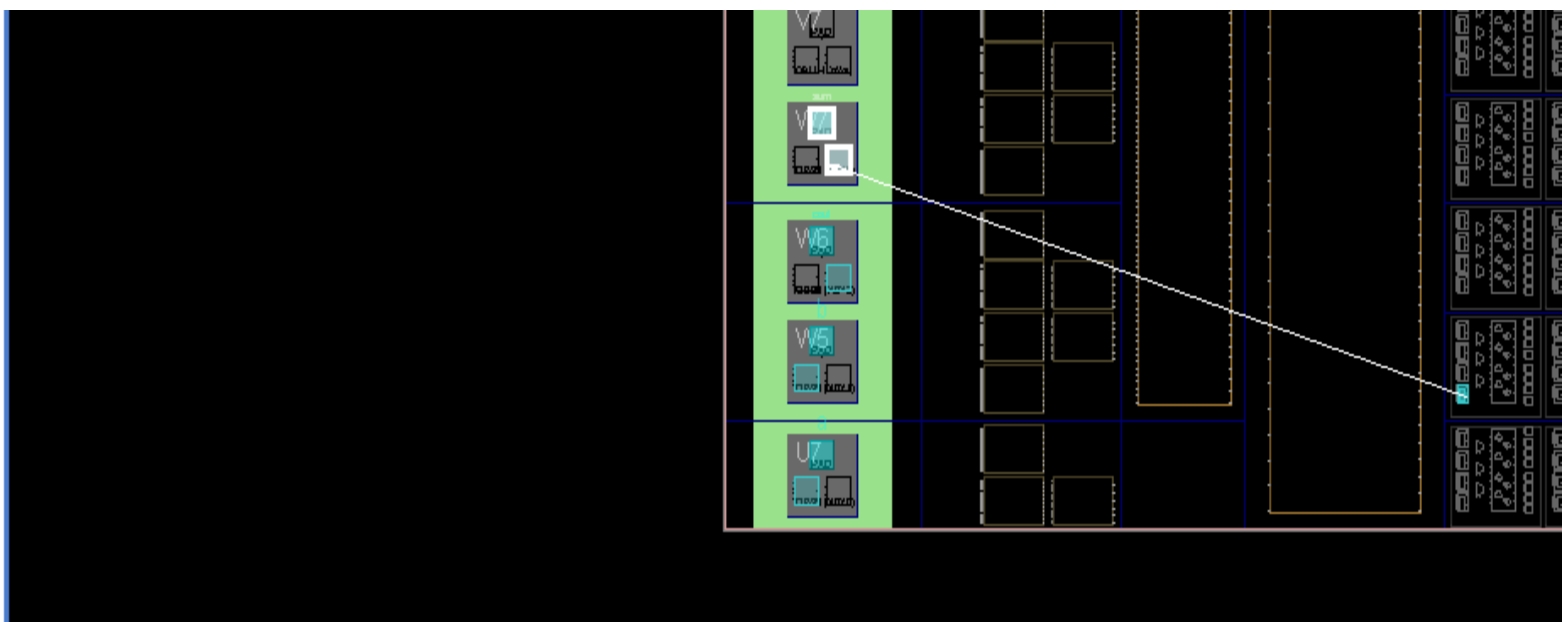

Leaf Cells (6)

- a\_IBUF\_inst (IBUF)
- b\_IBUF\_inst (IBUF)
- cout\_OBUF\_inst (OBUF
- cout\_OBUF\_inst\_i\_1 (L
- sum\_OBUF\_inst (OBU
- sum\_OBUF\_inst\_i\_1 (L


Cell Prop

cout\_OBUF\_inst\_i\_1

Name: cout\_OE



cout\_OBUF\_inst\_i\_1

 

# FPGA Advantages

- Long time availability
- Can be updated and upgraded at your customer's site
- Extremely short time to market
- Fast and efficient systems
- Performance gain for software applications
- Real time applications
- Massively parallel data processing