




Continuous Assessment Test II - May 2023

Programme	: B.Tech CSE	Semester	: Winter 2022-23
Course	: Digital System Design	Code	: BECE102L
Faculty	: A. Mohamed Imran	Slot	: B1+TB1
		Class Number	: CH2022232300550
Time	: $1\frac{1}{2}$ Hours	Max. Marks	: 50

Answer ALL Questions

 1. Design a sequential circuit using JK Flip Flop that implements the state diagram shown below.
- (a) Using binary assignment for the states, obtain the state table. (6)
  - (b) Find combinational circuit required for the inputs of the flip flops using k-maps. (6)
  - (c) Draw the sequential circuit. (3)



2. Design an asynchronous counter that counts 0,1,2,3 using D Flip Flop.
- (a) Draw the state table and the circuit required to implement the counter. (6)
  - (b) Verify the output using a timing diagram. (6)
  - (c) If the clock frequency is 64 kHz initially, what will be clock frequency for all other flip flops in the design. (3)

3. A serial input is sensed for a pattern 10011. Draw the state diagram to design a finite state machine using

(a) Moore Model and Overlapping bit pattern.


(5)

(b) Mealy Model and Non-Overlapping bit pattern.

(5)

4. Derive the state table and the state diagram of the sequential circuit shown below, where  $J$  is the input and  $R_1, R_2, A_1, A_2, G_1, G_2$  are the outputs. Consider only  $G_1$  as the output for building the state table and state diagram.

(10)

 

$$D_1 = (\overline{J} \cdot \overline{Q_2}) + \overline{Q_3}$$

$$D_2 = (\overline{J} \cdot \overline{Q_1}) + Q_3$$

$$D_3 = (Q_1 \cdot Q_3) + \overline{Q_2}$$

$$G_1 = \overline{Q_1} \cdot Q_3$$