

**VIT**

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

Continuous Assessment Test I – September 2023

Programme	: B.Tech.(ECE/ECM)	Semester	: FALL 2023-24
Course	: DIGITAL SYSTEM DESIGN	Code	: BECE102L
		Class Nbr	: CH2023240100538, CH2023240100368, CH2023240100369, CH2023240100535 CH2023240100365
		Slot	: B1+TB1
Faculty	: Dr Gargi Raina, Dr K Chitra, Dr B Lakshmi, Dr A Prathiba, Dr Jenifer	Max. Marks	: 50
Time	: 90 Minutes		

Answer ALL the questions

Q. No.	Sub. Sec.	Question Description	Marks
✓ 1	a)	Simplify the Boolean expression $\overline{A}\overline{B} + ABC + A(B + A\overline{B})$	[4]
	b)	Using K-map, simplify the following Boolean function and obtain i) minimal SOP and (ii) minimal POS expressions: $F = \sum_m(0, 2, 3, 6, 7) + \sum_d(8, 10, 11, 15)$	[6]
2	a)	The output of a circuit is 1 if a majority (more than half) of its inputs are equal to 1, and the output is 0 otherwise. Construct a truth table for a three-input majority circuit and design the circuit with NOR gates only	[6]
	b)	Construct the following logic expression using CMOS logic. $F = \overline{(A + B + C).D}$	[4]
✓ 3	a)	Specify the number of registers and the number of bits per register in the following statement: reg [0:7] name [0:4];	[1]


b) Find the output of the test bench shown

[5]

```
//dataflow half_adder test bench module
half_adder_df_tb;
reg a, b;
wire sum, cout;
initial
$monitor ("ab = %b, sum = %b, cout = %b", {a, b}, sum, cout);
initial
begin
#10  a = 1'b0;
      b = 1'b0;
#10  a = 1'b0;
      b = 1'b1;
#10  a = 1'b1;
      b = 1'b0;
#10  a = 1'b1;
      b = 1'b1;
#10 $stop;
end
half_adder_dfinst1 (.a(a), .b(b), .sum(sum), .cout(cout) );
endmodule
```

c) Write a Verilog HDL code for the schematic shown

[4]

 

4 a) Assume that the exclusive-OR gate has a propagation delay of 10 ns and that the AND/OR gates have a propagation delay of 5 ns. What is the total propagation delay time for the full adder circuit? Draw the circuit used for calculation

[3]

b) Draw the logic diagram of a 2-to-4-line decoder using universal NAND gates. Include an enable input.

[2]

c) Implement the following Boolean function with a 4 X 1 multiplexer and external gates.

[5]

$$F1(A, B, C, D) = \sum (1, 3, 4, 11, 12, 13, 14, 15)$$

5. Design a 4-input priority encoder and simulate the same using Verilog code with gate primitives. Assume that input D3 has the highest priority

[10]

Total [50]